

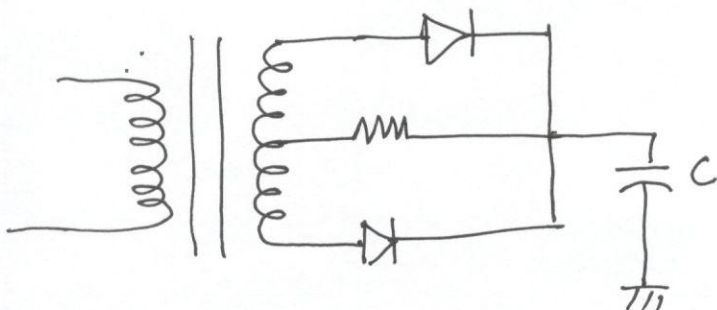
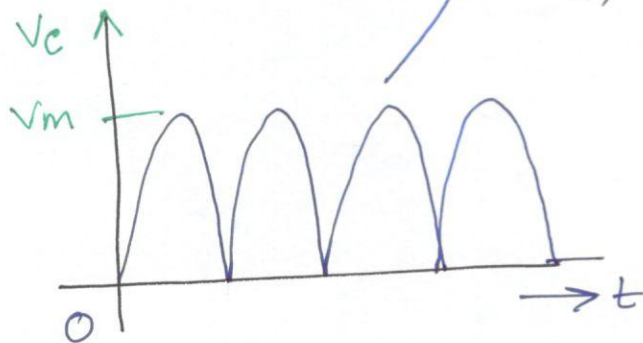
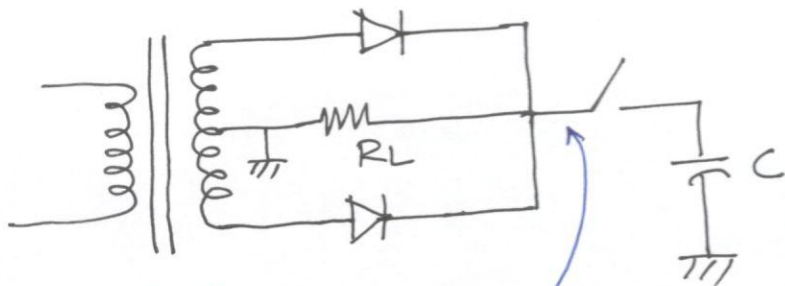


Capacitor Filter


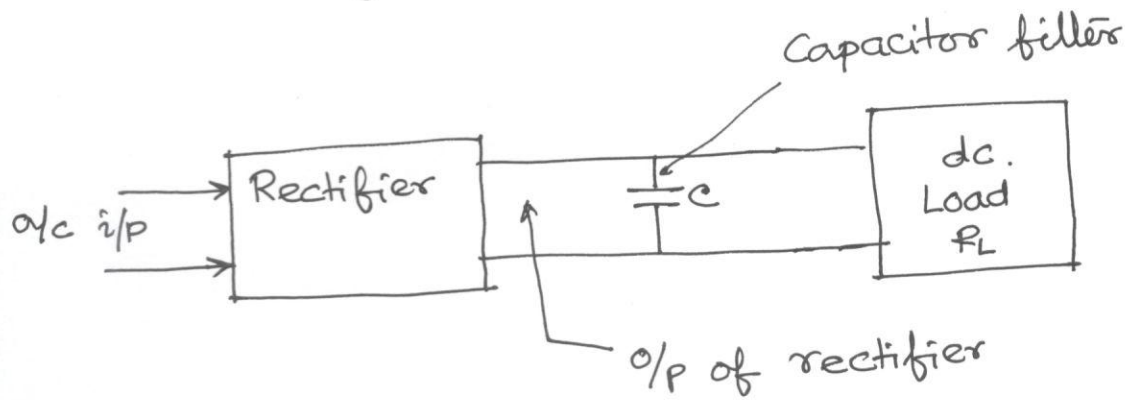
A capacitor is connected at rectifier output. d.c. voltage is obtained across the capacitor.



Full wave rectifier.

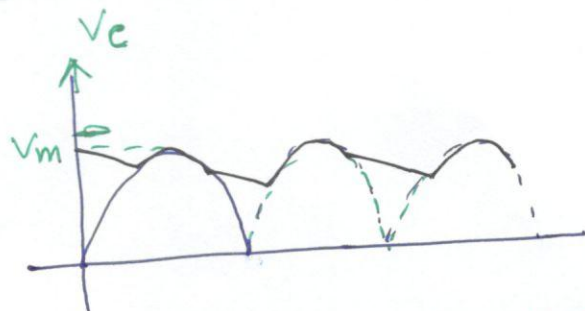

Filtered o/p voltage

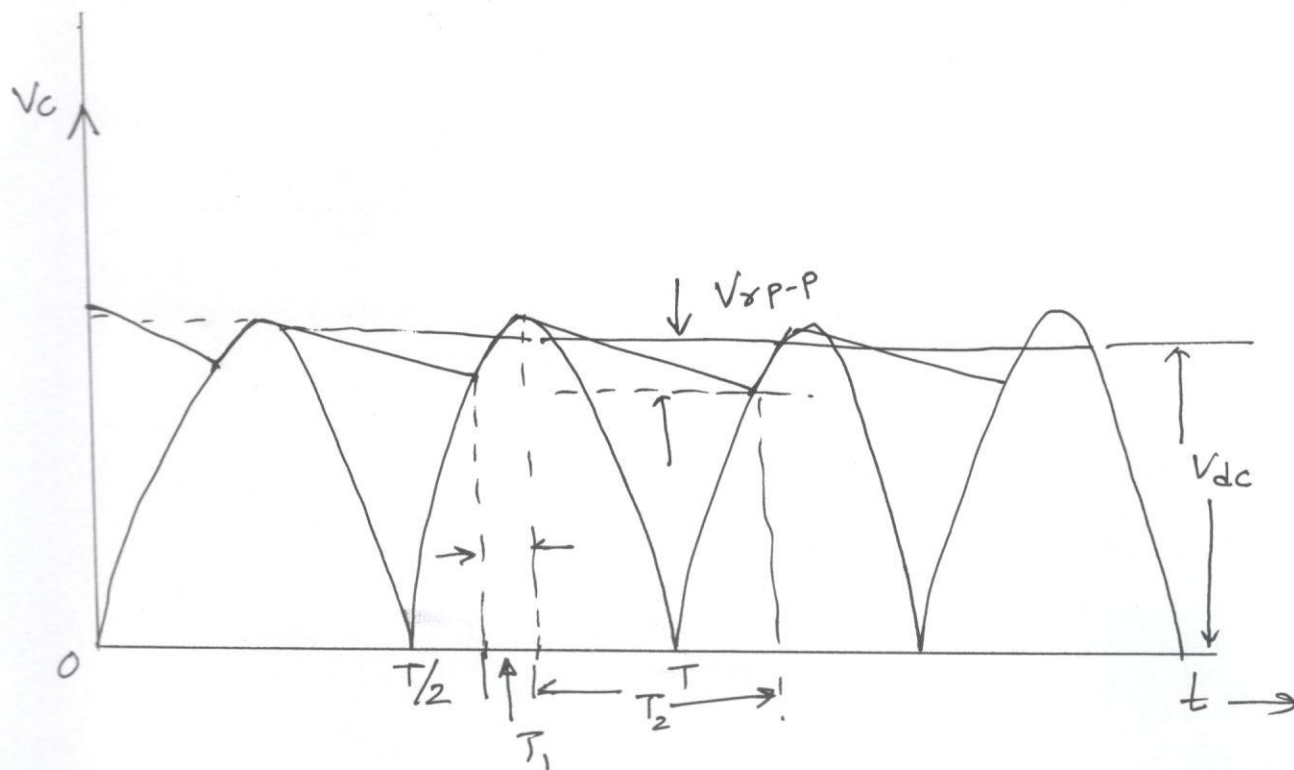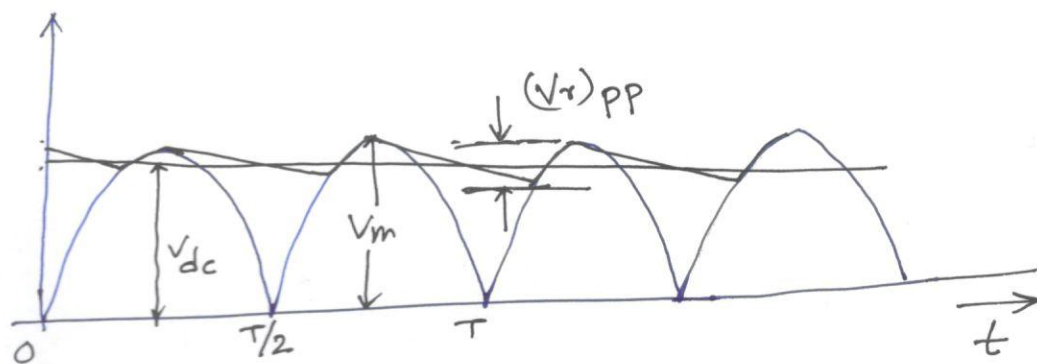

ripple voltage

$$V_r(\text{rms}) = \frac{I_{dc}}{4\sqrt{3} fc} = \frac{2.4 I_{dc}}{C}$$

$$= \frac{2.4 V_{dc}}{R_L C}$$

I_{dc} : milliamp.

C : microfarad

R_L : Kilo Ω

T_1 : diode conducts and charges C to V_m

T_2 : Rectifier voltage drops below the peak and capacitor discharges through load.

Avg ct drawn from the supply = avg
of the ct through the diode during charging

$$I_{dc} \cdot T = I_p \cdot T_1$$

$$\text{or } I_{\text{peak}} = I_p = I_{dc} \frac{T}{T_1}$$

T_1 : Diode conduction time

$$T = 1/f$$

Small $C \Rightarrow$ large conduction time of diode
 \Rightarrow peak ct not very high

Large $C \Rightarrow$ small conduction time
 \Rightarrow very high ~~pick~~ peak ct.
(Diode peak ct)


$$I_{dc} \cdot T = I_p \cdot T_1$$

$$I_p = I_{dc} \cdot \frac{T}{T_1}$$

$$V_{dc} = V_m - \frac{I_{dc}}{4fC} = V_m - \frac{4.17 I_{dc}}{\pi C}$$

$$T = 1/f \quad f = \frac{2 \times 60}{1} = 120 \text{ Hz}$$


f : ripple frequency for F.W

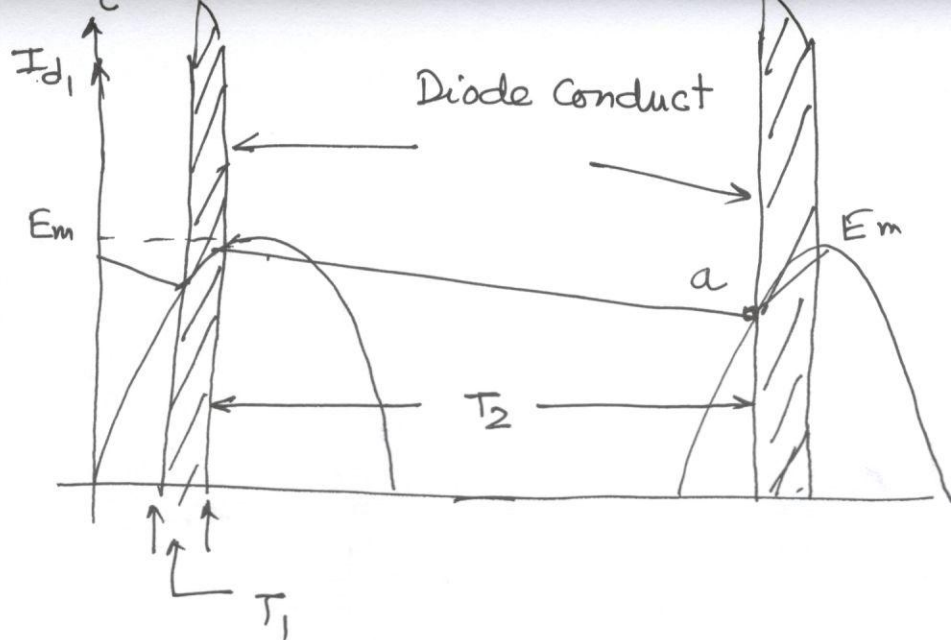




- For time T_1 diode conducts and charges the capacitor to E_m
- After this capacitor discharges for T_2 when the voltage across C falls below rectified voltage, say at a point a , the diode conduction starts and C is charged to E_m .
- The average αt supplied to the capacitor and load must be $=$ avg αt drawn from the capacitor during T_2 .
- Diode conducts for small period of time
- Larger the $C \Rightarrow$ less the voltage decay \Rightarrow shorter the interval of charging.
But diode has to supply same avg αt
 \Rightarrow peak αt increases.

RC Filter

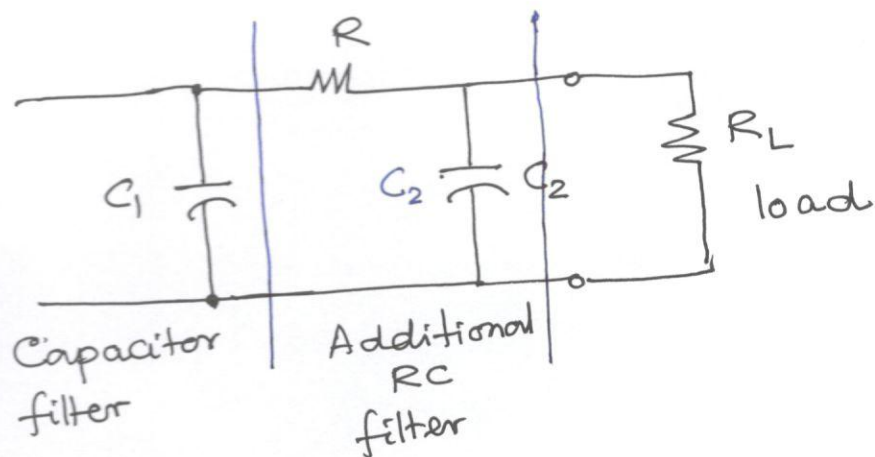
- It is possible to further reduce the amount of ripple across a filter capacitor by using an additional RC filter.



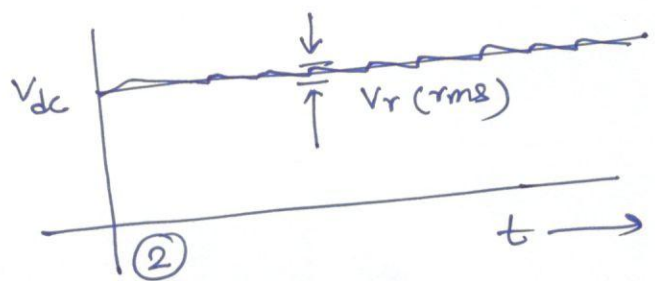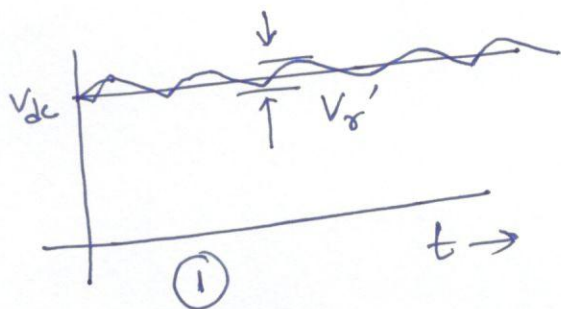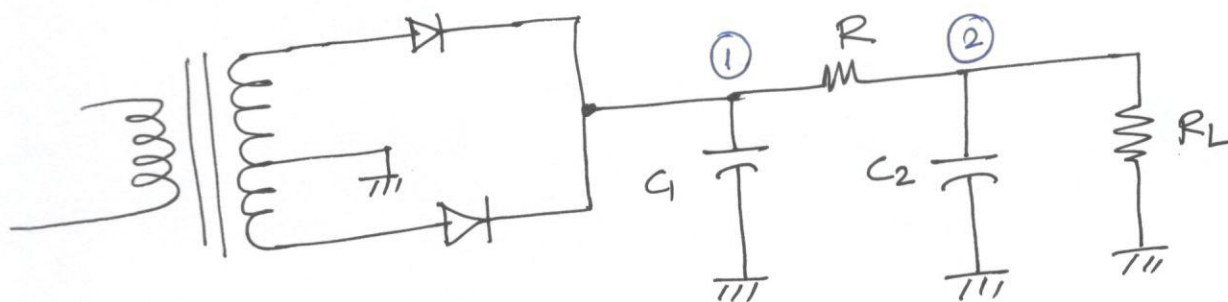- The added RC section passes most of the d.c. component while attenuating as much as the a.c. component




DC operation of RC Filter Section

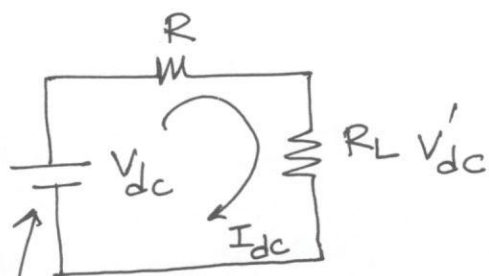

D.C. voltage developed across

C_1
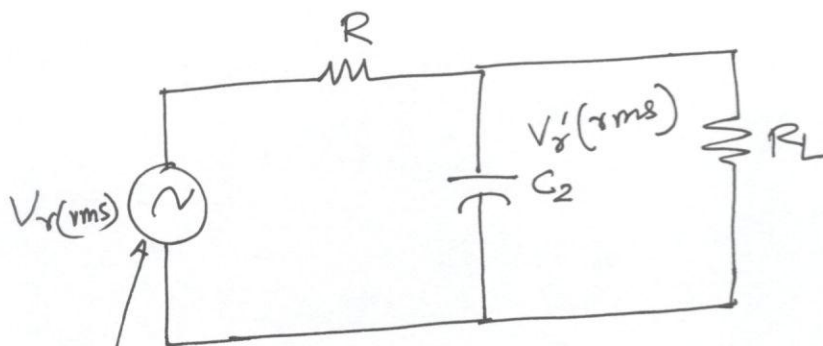
$$V'_{dc} = V_{dc} \cdot \frac{R_L}{(R + R_L)}$$



A.C. ripple voltage developed across C_1

$$V'_r(rms) \approx \frac{X_C}{R} V_r(rms)$$

$V'_r(rms)$: A.C. Component of voltage across load.

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 120 \times C} = \frac{1.3}{C}$$

X_C is in $k\Omega$, if C is in μF .