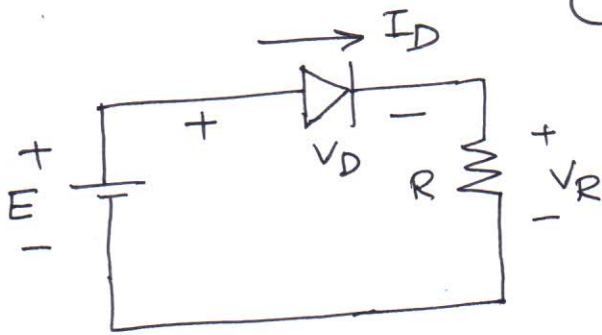


# Load Line analysis for Diode

(Quiescent point, Q-pt)




Applying Kirchhoff's voltage law to the ckt

$$-E + V_D + V_R = 0$$


$$\text{or } E = V_D + V_R$$

$$V_R = I_D \cdot R$$

$$\text{so } E = V_D + I_D R.$$

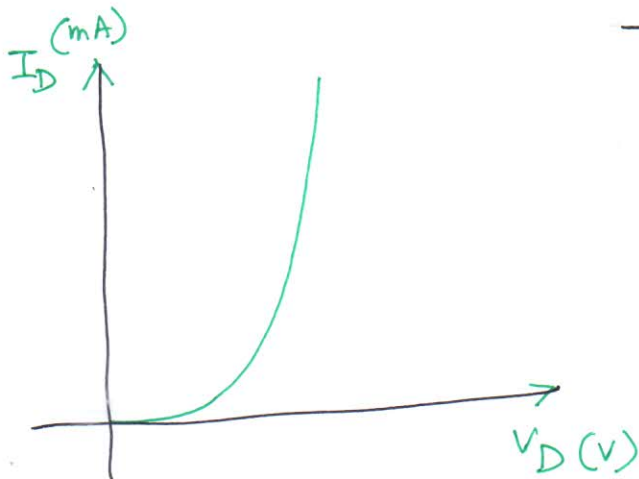

Diode characteristic

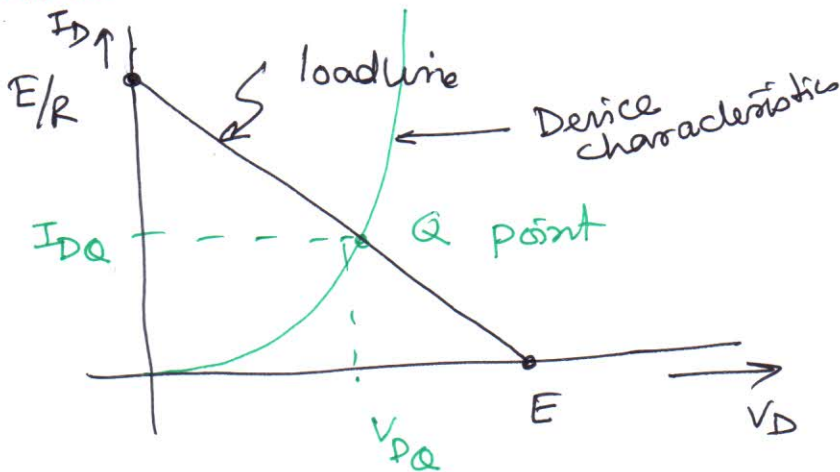

$$I_D = 0 \\ E = V_D$$

$$V_D = 0, \\ I_D = E/R$$

$$V_D = E \mid I_D = 0$$

$$I_D = E/R \mid V_D = 0$$


Slope of the load

line ~~is~~ depends on R.

point of intersection of load line and device characteristic is the Q point.

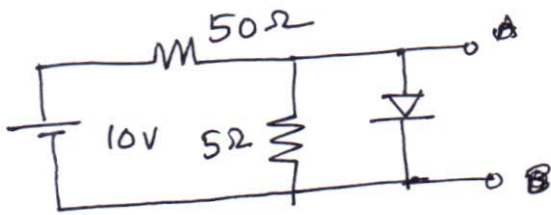
## Problems

Ex: 1. Find the current through the diode in the ckt shown in the Fig. Assume the diode as ideal.




The diode will be forward biased.
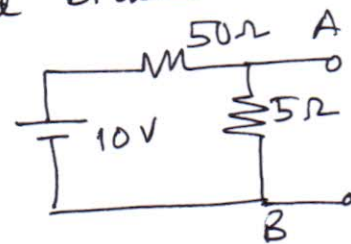
$$V_{AB} = \frac{10 \times 5}{50 + 5} = \frac{10}{11}$$



When the Diode is forward biased (S.C).

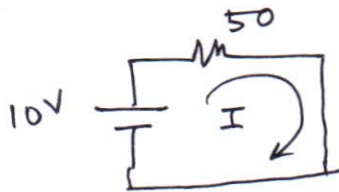


$$I = \frac{10V}{50\Omega} = 0.2A$$

Ex:-2. Two identical diodes are connected as shown, with following characteristics

$$I_S = 0.1 \mu A \quad V_T = 26 mV \quad \eta = 2$$

$$\text{Supply voltage} = 15V \quad R_L = 100k$$

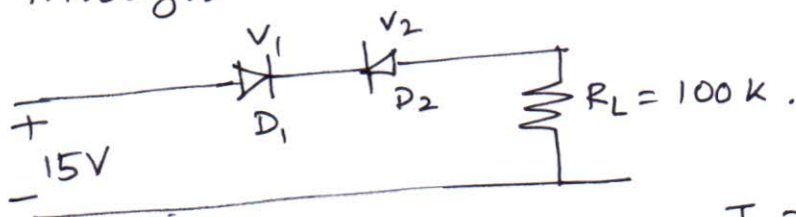Find the voltage across each diode and current through the ckt.



$D_1$  : fwd biased  
ct through  $D_1$

$$I_1 = I_0 \left( e^{\frac{qV_1}{nKT}} - 1 \right)$$



$D_2$  is reverse biased, so current through it is  $I_0$ .

$$I_1 = I_0$$

$$I_0 \left( e^{\frac{qV_1}{\eta kT}} - 1 \right) = I_0$$

$$\text{or, } e^{\frac{qV_1}{\eta kT}} = 2$$

$$\text{or, } V_1 = \left( \frac{\eta kT}{q} \right) \ln 2$$

$$= 2 \times 26 \times \ln 2 \text{ mV} = 0.036 \text{ V}$$

$$V_2 = V - V_1 = 15 - 0.036 = 14.964 \text{ V}$$