
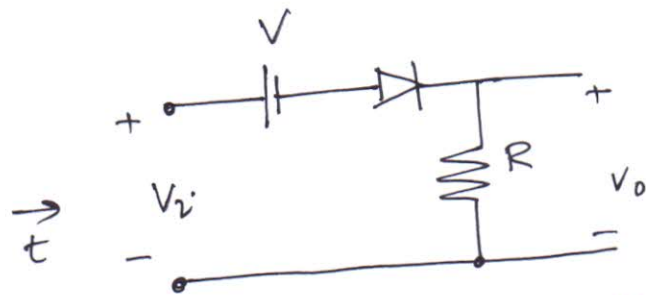
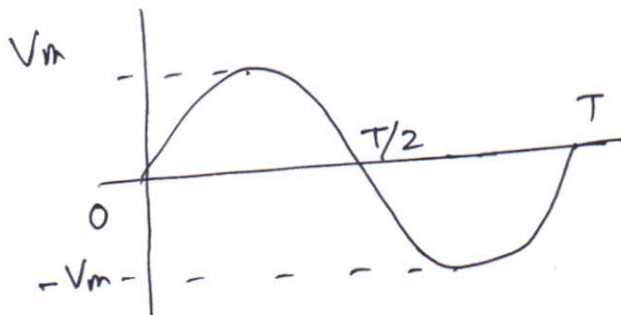
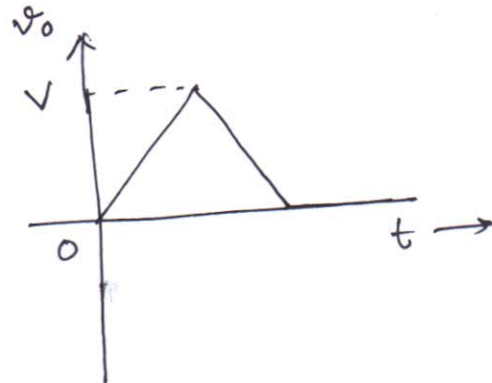
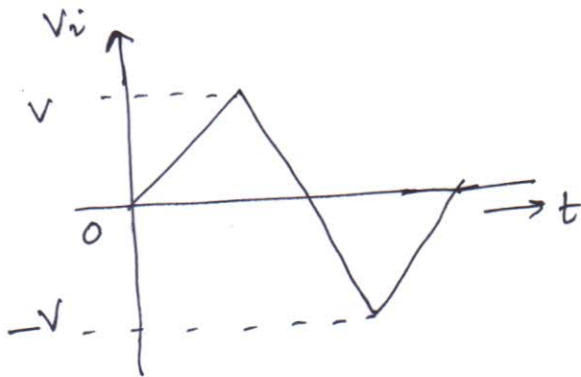
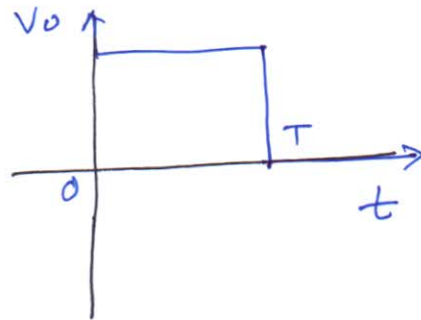
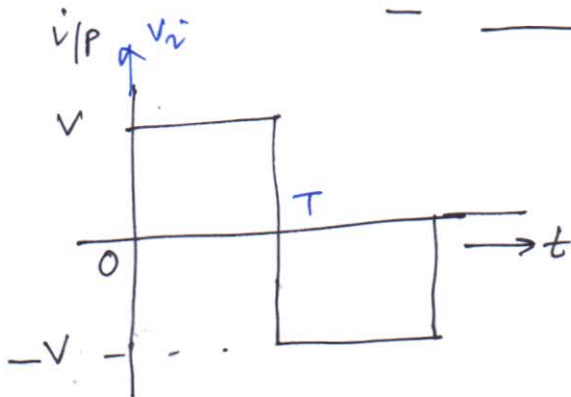


# CLIPPERS

"CLIP" OFF PORTION OF THE I/P SIGNAL  
WITHOUT DISTORTING REMAINING PART OF THE  
AC WAVEFORM.


Series.

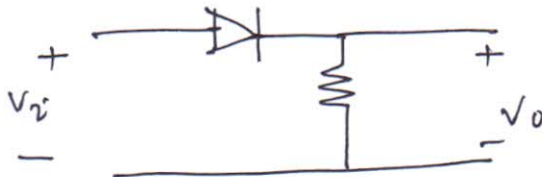

- Make a sketch of response of N/W based on direction of diode and applied voltage
- Determine applied voltage (transition voltage) that causes a change in state of Diode.

For the ideal diode transition occurs at  $i_D = 0$ ,  $V_D = 0$

- Apply this condition to the network.

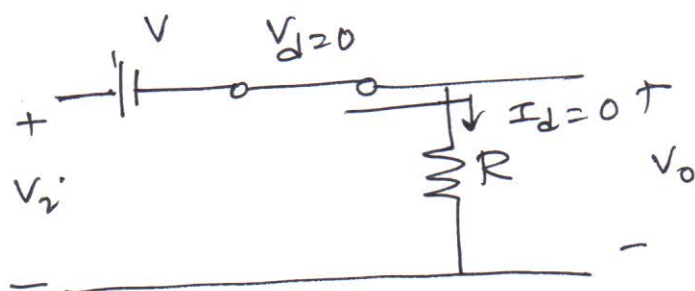

$$V_o = I_R \cdot R = I_D \cdot R = 0$$


$$V_o = 0$$

$$V_i = V$$

So level of  $V_i = V$  will cause a change/transition in state.



- Thus for an i/p voltage greater than  $V$ , diode is in short-ckt state, while for i/p less than ' $V$ ' volt, it is in open ckt or OFF state.

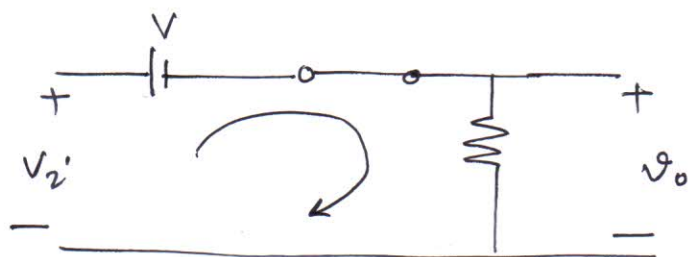- When the diode is in short ckt state, the o/p voltage  $V_o$  can be determined by KVL





$$-V_i + V + V_o = 0$$

$$\text{or } V_o = V_i - V$$

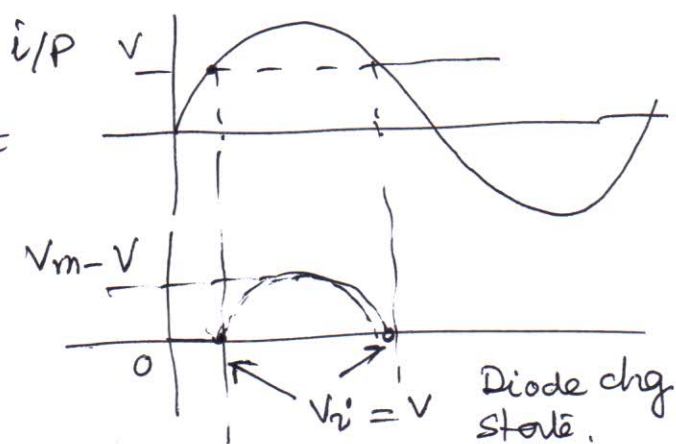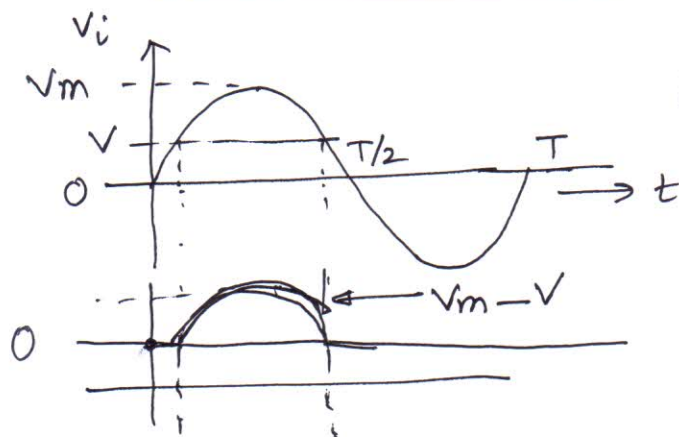


Ex:

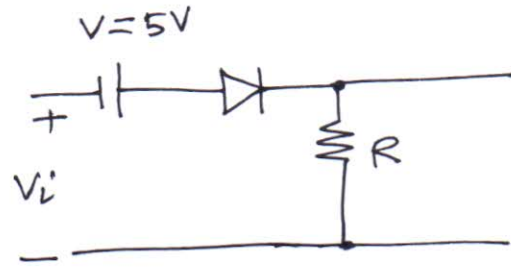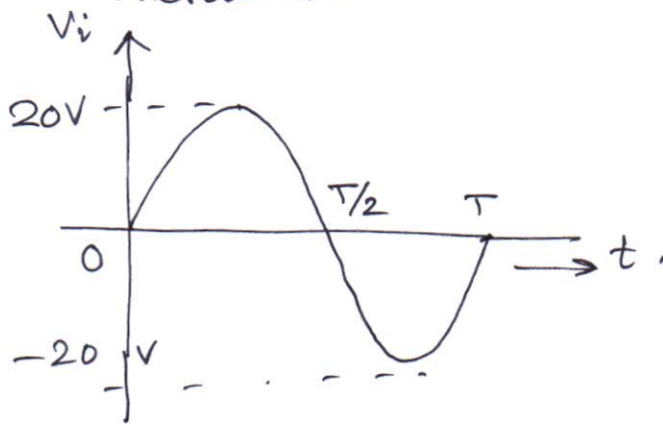Determine the o/p waveform of the Network.



Diode will be ON for +ve  $V_i$

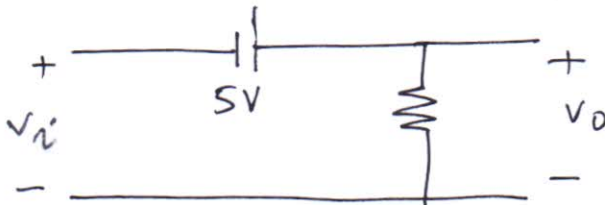

$$-V_i - 5 + V_o = 0$$

or  $V_o = V_i + 5$


For transition level,




$$V_d = 0, \quad i_d = 0$$

$$-V_i - 5 = 0$$

$$V_i = -5V$$

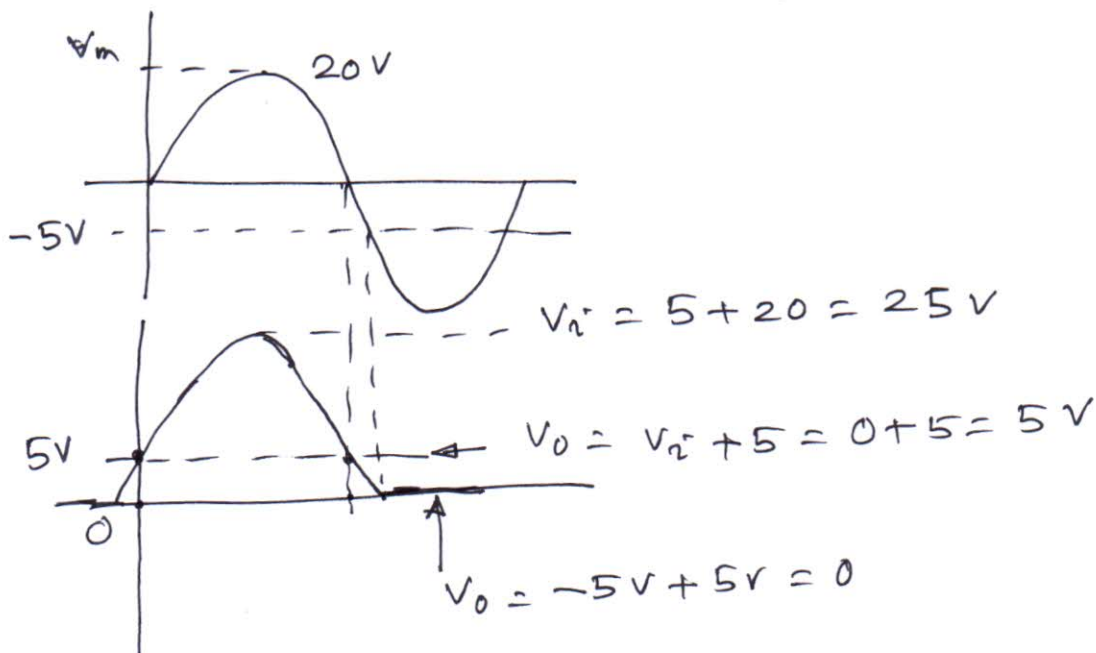For  $V_i$  more negative than  $-5V$ , Diode is OFF  
 For  $V_i$  more +ve than  $-5V$ , Diode is ON



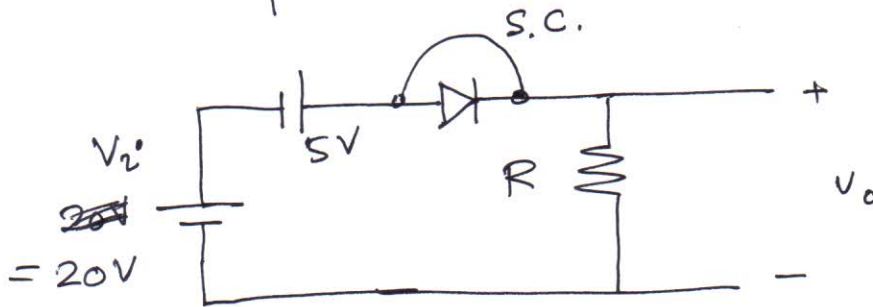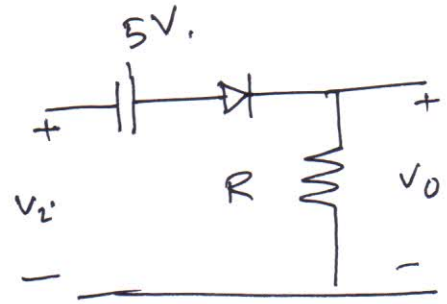
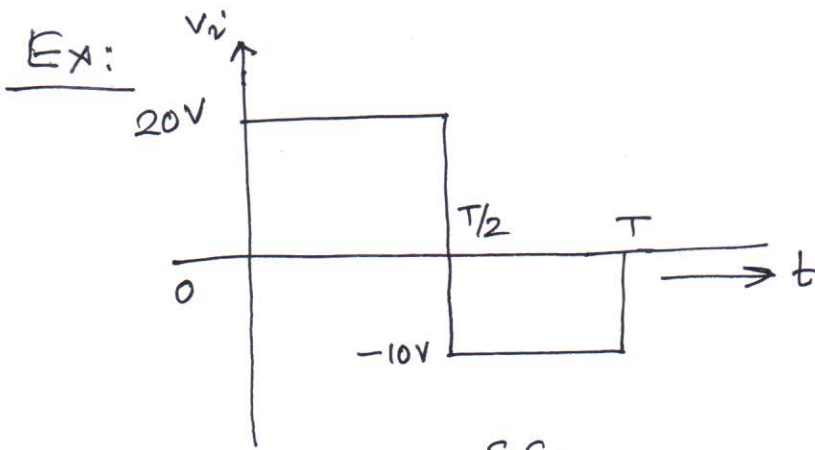


For  $v_i = 20V$  ( $0 \rightarrow T/2$ ), Diode is S.C.

$$v_o = 25V.$$






For  $v_i = -10V$ , Diode is OFF / O.Ckt.

$$v_o = 0V.$$

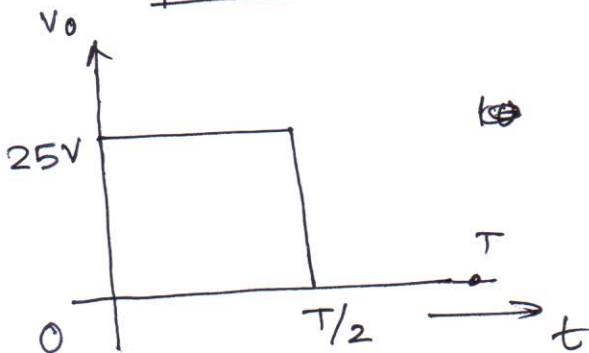
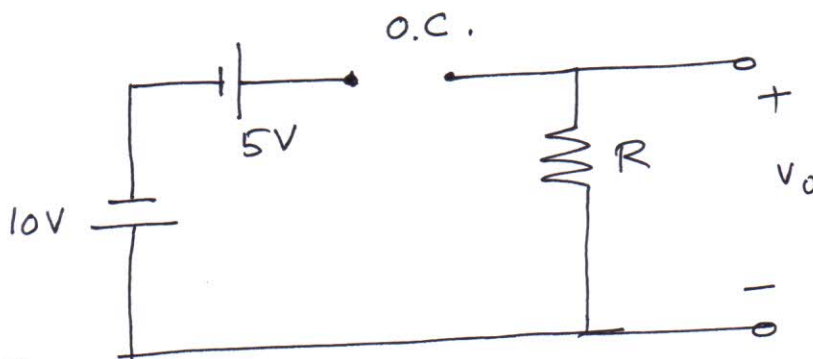


$$v_o = 0V.$$

Parallel

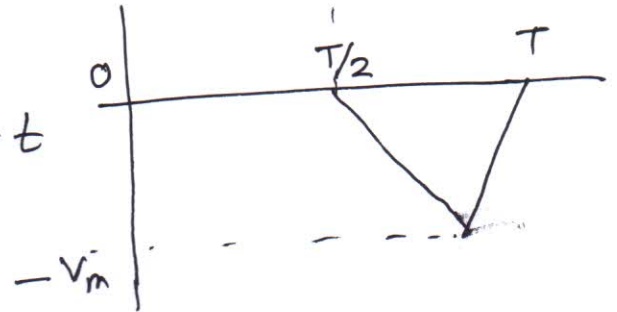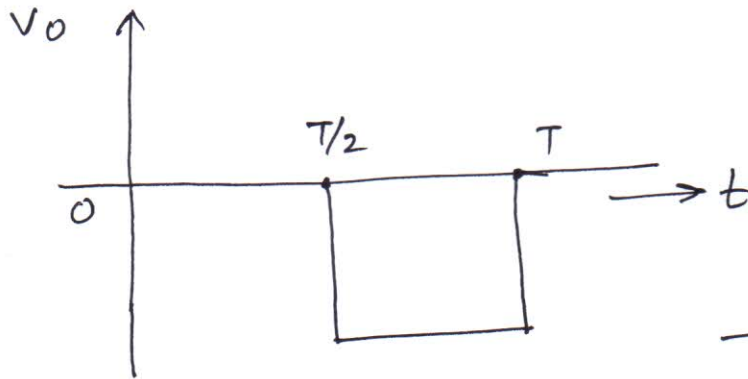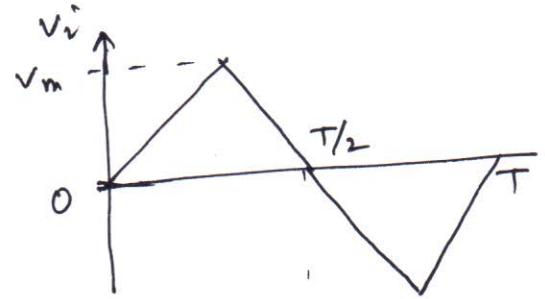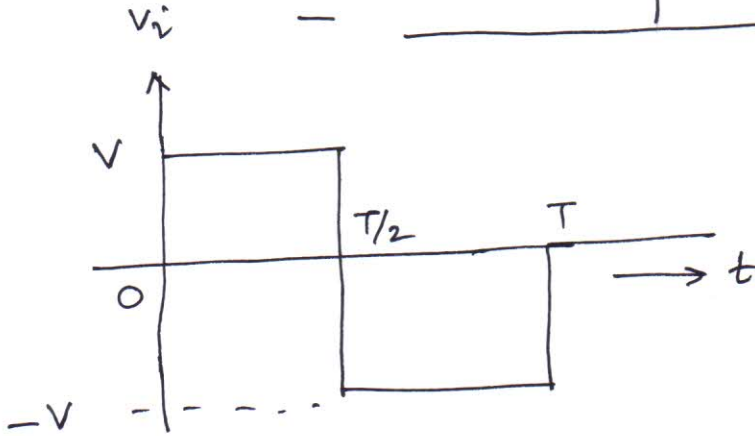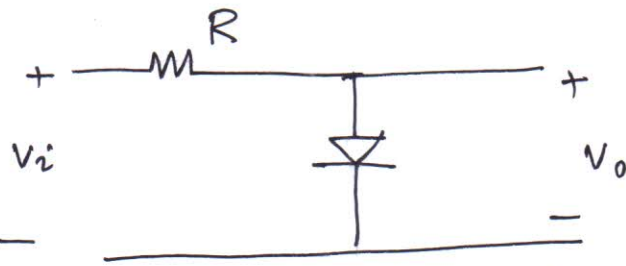


Ex:

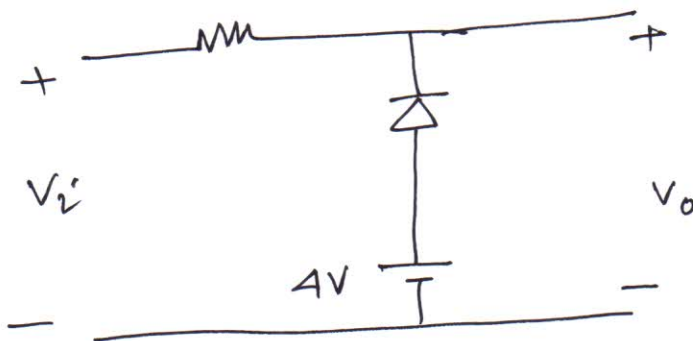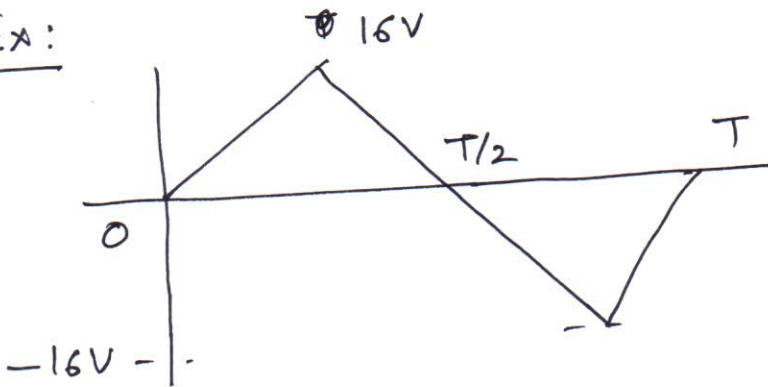




Diode will be ON for -ve region of i/p.

Network appears as

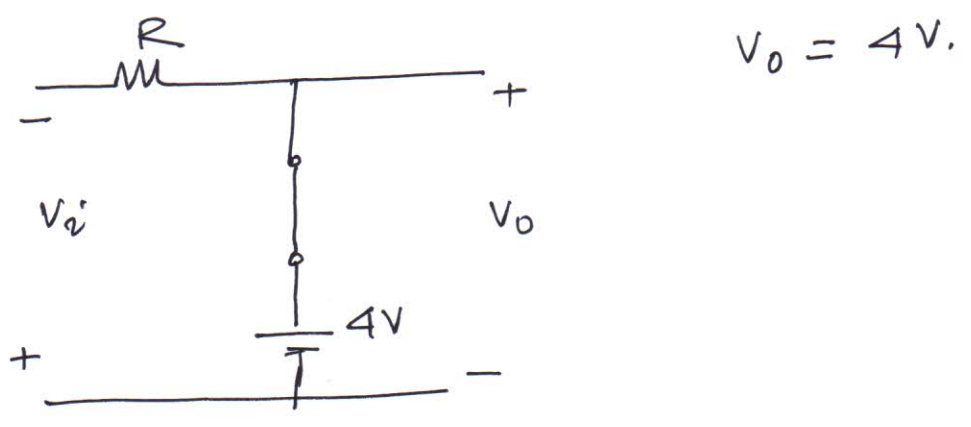


transition state  
 $V_d = 0, i_d = 0$

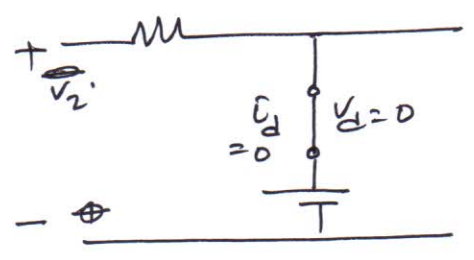

$$-V_i + 4 = 0$$
$$V_i = 4V.$$

i/p  $V_i > 4V$   
 $V_i < 4V$

Diode goes OFF  
Diode is ON.

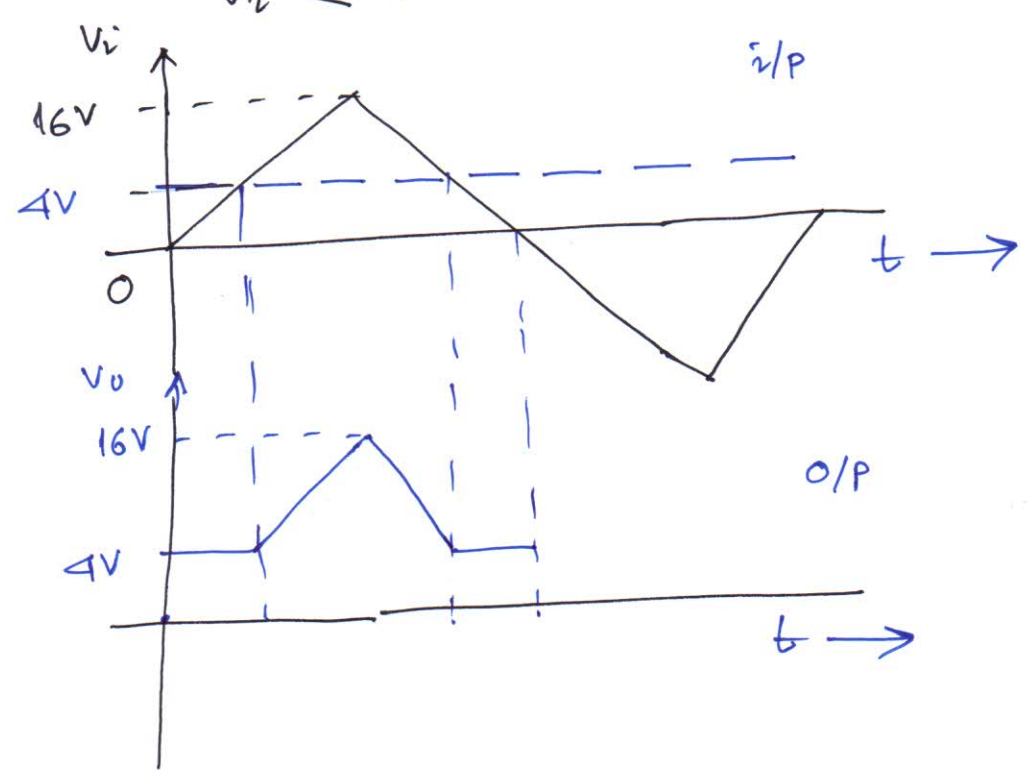




## CLAMPERS

The clamping network will 'clamp' a signal to a different d.c. level.

The Network will have a Capacitor, diode, resistor.

It can have an independent d.c. supply to introduce additional shift.

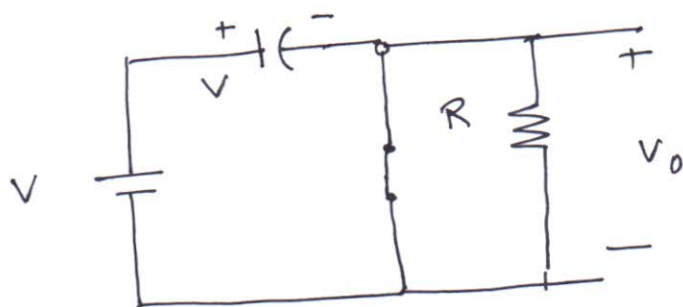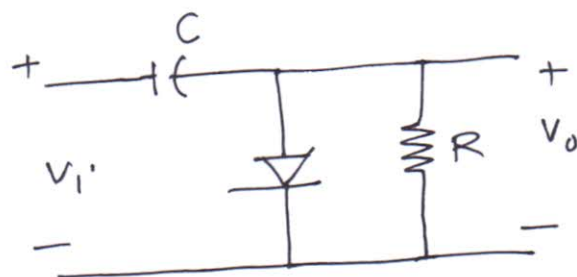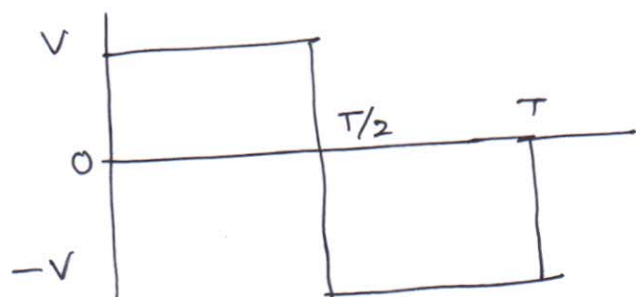
$R$  &  $C$  chosen such that  $\tau = RC$  is large enough to ensure that the voltage across the capacitor does not discharge significantly, during the interval when diode is non-conducting.



$$V_o = 0 \text{ V}$$

during  $0 \rightarrow T/2$


$C$  charges to  $V$  quickly

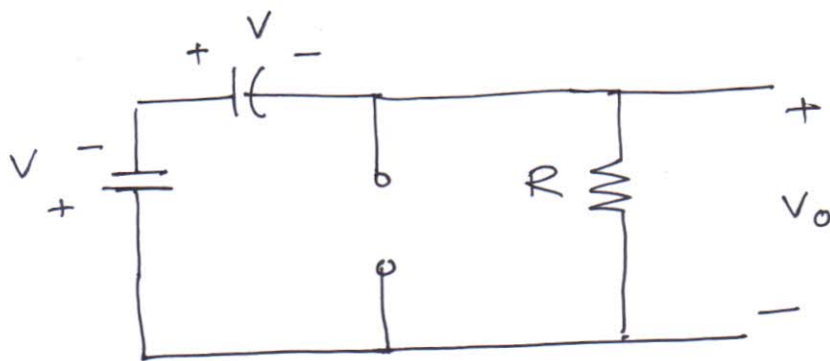

$$V_o = -2V.$$

O/p wave form.

$$V_o = -2V.$$

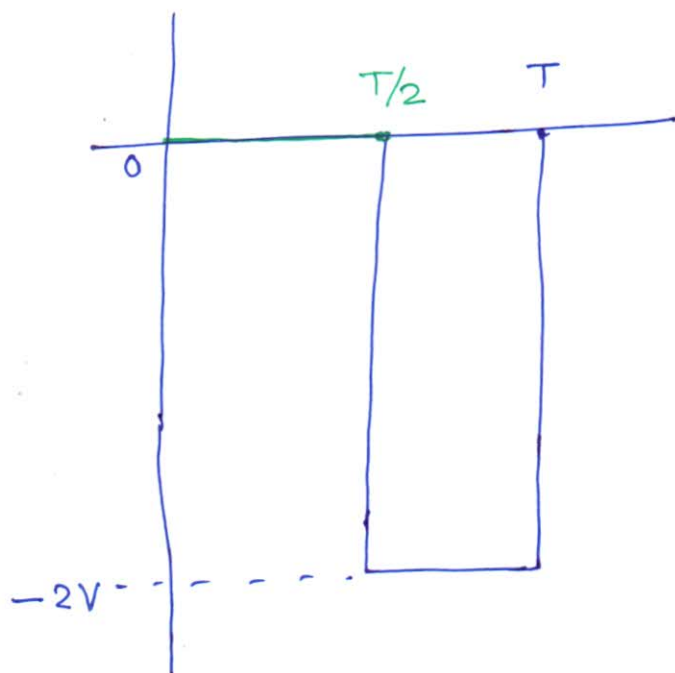

$RC$  product is sufficiently large to establish a discharge period of  $5\tau$  much greater than  $T/2 \rightarrow T$ , Capacitor holds onto all its charge and therefore, voltage ( $V = Q/C$ ) during this period.


$$+V + V + V_o = 0$$

$$\text{or, } V_o = -2V.$$


Total swing of O/p  
= Total swing of i/p



Ex:

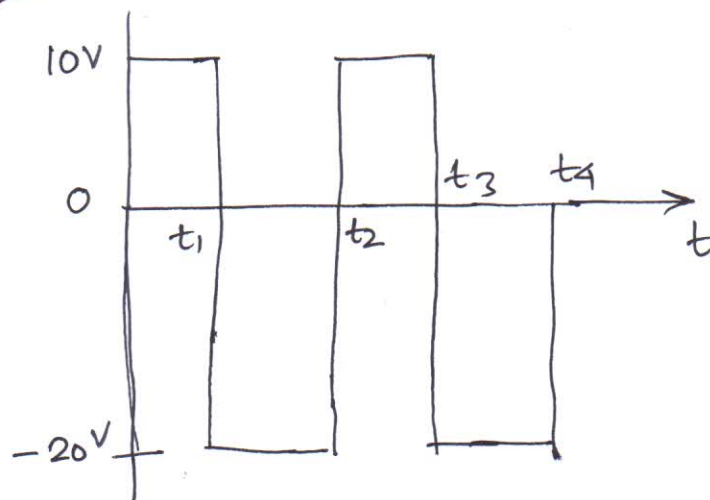

$$f = 1000 \text{ Hz}$$

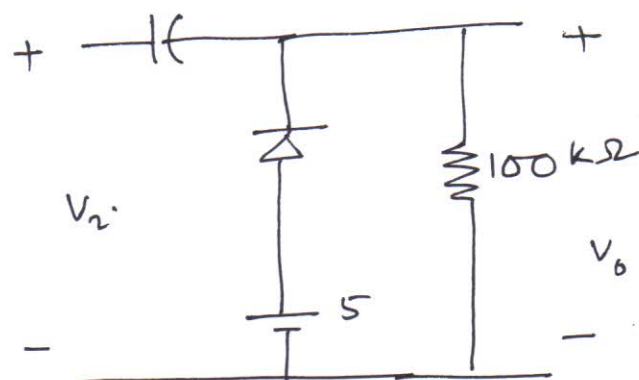


Step-1  $0 - t_1 = 0.5 \text{ ms}$

$f = 1000 \text{ Hz}$  period = 1 ms.

- Start the analysis by considering that part of i/p signal which will fwd bias the diode

So we start  $t_1 \rightarrow t_2$

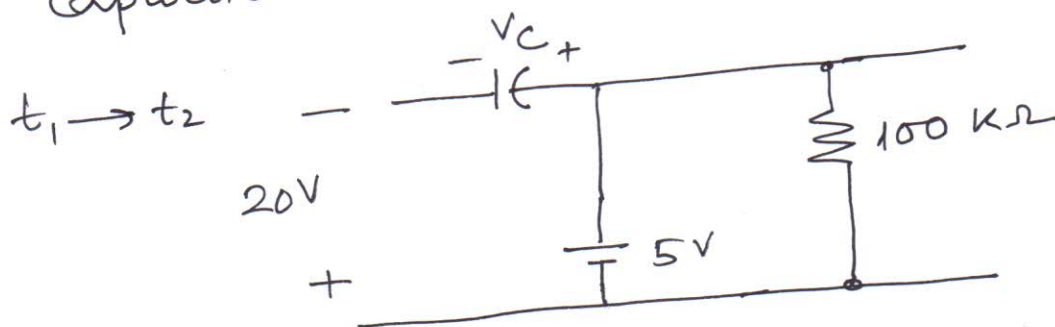- During the period when diode is 'ON' capacitor will charge up instantaneously.
- During the period when diode is 'OFF' capacitor holds on its voltage level.




$$20 - V_C + 5 = 0$$

$$V_C = 25 \text{ V}$$

Capacitor charges upto 25 V.

$$V_O = 5 \text{ V}$$

$t_1 \rightarrow t_2$

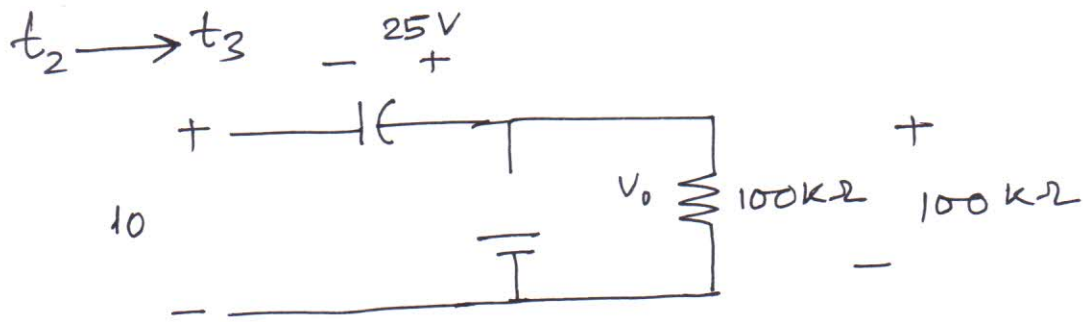

$$-10 - 25 + V_0 = 0 \quad \Rightarrow \quad V_0 = 35V \quad t_2 - t_3, V_0 = 35V$$

Time const for the discharging n/w

$$\tau = RC = 100 \times 10^3 \times 0.1 \times 10^{-6} = 10 \text{ ms}$$

$$R = 100 \text{ k}\Omega \quad C = 0.1 \mu\text{F}$$

$$\text{total discharge time} = 5\tau = 50 \text{ ms}$$

