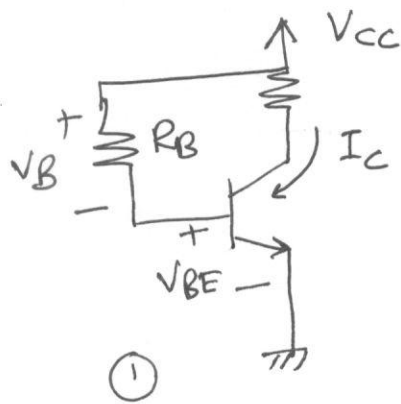



Explanation of stability w.r.t I_{CO}

①




Fixed Bias.

①

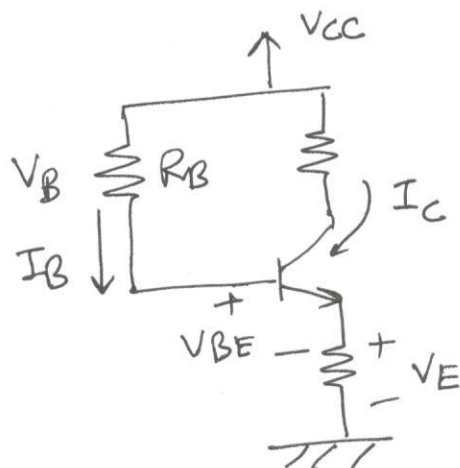

② Emitter Bias

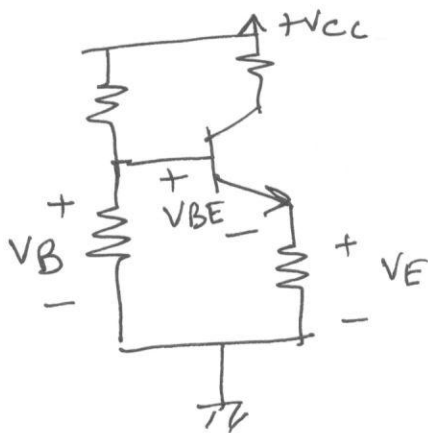


$$① \quad I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B + (\beta + 1) I_{CO}$$

Due to increase in I_{CO} , I_C increases,
there is nothing in the eqn for I_B that
would attempt to offset this undesirable
increase in it level. (assuming V_{BE} is const)
 I_C will continue to rise with temp, I_B remains const.

Emitter Bias

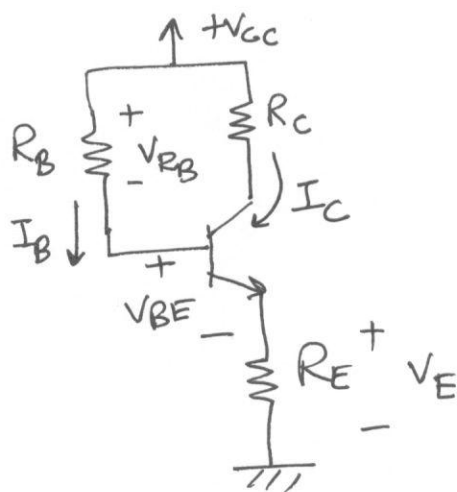

$$I_B = \frac{V_{CC} - V_{BE} - V_E}{R_B}$$

as $V_E \uparrow, I_B \downarrow$

Increase in I_C due to (\uparrow in I_{C0}) will cause voltage $V_E = I_E R_E \approx I_C R_E$ to increase.


This will cause I_B to drop as

$$I_B \downarrow = \frac{V_{CC} - V_{BE} - V_E \uparrow}{R_B}$$

A drop in I_B will have the effect of reducing the level of I_C through transistor action and thereby offset the tendency of I_C to increase due to an increase in temp.

Thus there is a reaction to an increase in I_C that will tend to oppose the change in bias conditions.

(3)

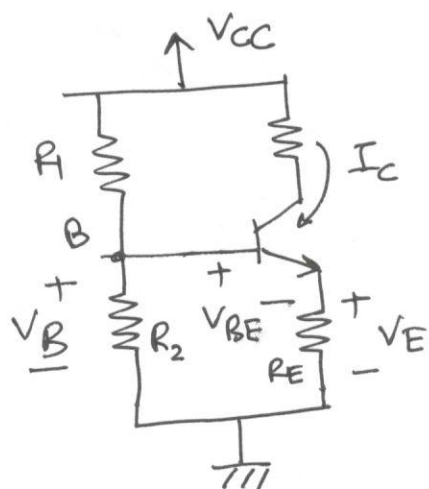

Voltage - divider bias.

If $\beta R_E \gg 10 R_2$ is satisfied, the voltage V_B will remain fairly constant for changing level of I_C .


$$V_{BE} = V_B - V_E,$$

If I_C should increase, V_E will increase,

V_{BE} will \downarrow , for a constant V_B .

As $V_{BE} \downarrow$, $I_B \downarrow$ which will try to offset the increased level of I_C .

④


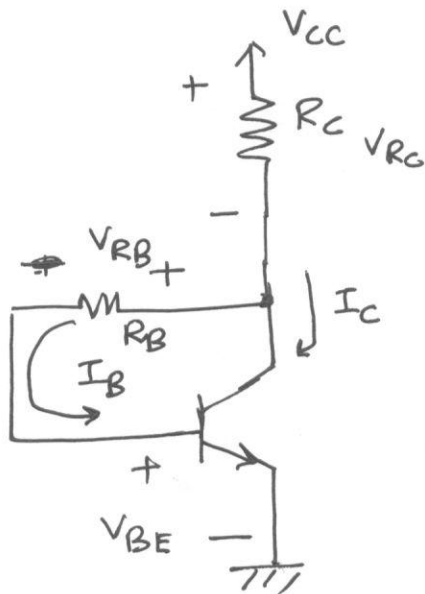


Collector Feedback Config

$$I_B \downarrow = \frac{V_{CC} - V_{BE} - V_{RC} \uparrow}{R_B}$$

An increase in I_C due to increase in temp,
causes V_{RC} to increase \uparrow .
and as a result $I_B \downarrow$ as seen in the eqn.

①

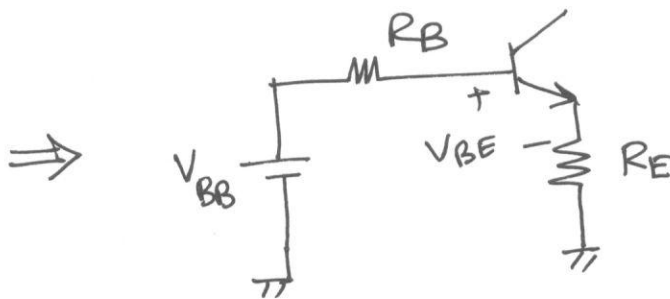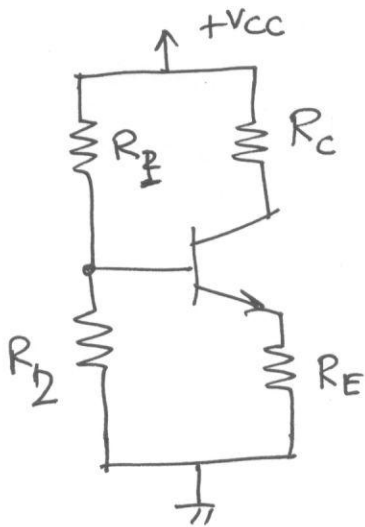Derivation of $s(\beta)$ 

$$R_B = R_1 \parallel R_2$$

$$V_{BB} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$I_C = \beta I_B + (\beta + 1) I_{CB0}$$

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E \quad \text{(a) using KVL in Base-Emitter loop}$$

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E :$$

↑ using KVL in Collector-Emitter loop

$$I_C = \alpha I_E + I_{CB0}$$

$$I_E = I_B + I_C$$

$$\text{or } I_B = \frac{1 - \alpha}{\alpha} I_C - \frac{I_{CB0}}{\alpha} = (1 - \alpha) I_E - I_{CB0}$$

$$= \frac{I_E}{(\beta + 1)} - I_{CB0} \quad \text{(b)}$$

$$I_B = \frac{I_E}{(\beta+1)} - I_{CBO}$$

$$I_C = \frac{\beta I_E}{(\beta+1)} + I_{CBO} \quad \text{--- (c)}$$

Combining (a) & (b)

$$V_{BB} = V_{BE} - I_{CBO} R_B + I_E \left(R_E + \frac{R_B}{\beta+1} \right)$$

Now use eqn (c) to obtain

$$I_{CQ} = \frac{\beta (V_{BB} - V_{BE}) + (\beta+1) I_{CBO} (R_E + R_B)}{(\beta+1) R_E + R_B}$$

To calculate S_β

Since $V_{BB} - V_{BE} \gg I_{CBO} (R_E + R_B)$ in Active region, the I_{CBO} term is neglected.

$$\text{Thus } I_{CQ} \approx \beta \frac{(V_{BB} - V_{BE})}{R_B + (\beta+1) R_E}$$

Let β_1 and β_2 are two values on β with I_{CQ_1} and I_{CQ_2} are corresponding currents.

Next we form the ratio

$$\frac{I_{CQ2}}{I_{CQ1}} = \frac{\beta_2}{\beta_1} \left[\frac{R_B + (\beta_1 + 1)R_E}{R_B + (\beta_2 + 1)R_E} \right]$$

$$\frac{I_{CQ2} - I_{CQ1}}{I_{CQ1}} = \frac{\Delta I_{CQ}}{I_{CQ1}} = \frac{\Delta \beta (R_B + R_E)}{\beta_1 [R_B + (\beta_2 + 1)R_E]}$$

$$\Delta I_{CQ} = I_{CQ2} - I_{CQ1} \quad \Delta \beta = \beta_2 - \beta_1$$

$$\text{Thus } S_\beta = \frac{\Delta I_{CQ}}{\Delta \beta} = \frac{I_{CQ1}}{\beta_1} \left[\frac{R_B + R_E}{R_B + (\beta_2 + 1)R_E} \right]$$

For Emitter - Bias Configuration

$$S(\beta) = \frac{\Delta I_C}{\Delta \beta} = \frac{I_{C1} (1 + R_B/R_E)}{\beta_1 (\beta_2 + R_B/R_E)}$$

