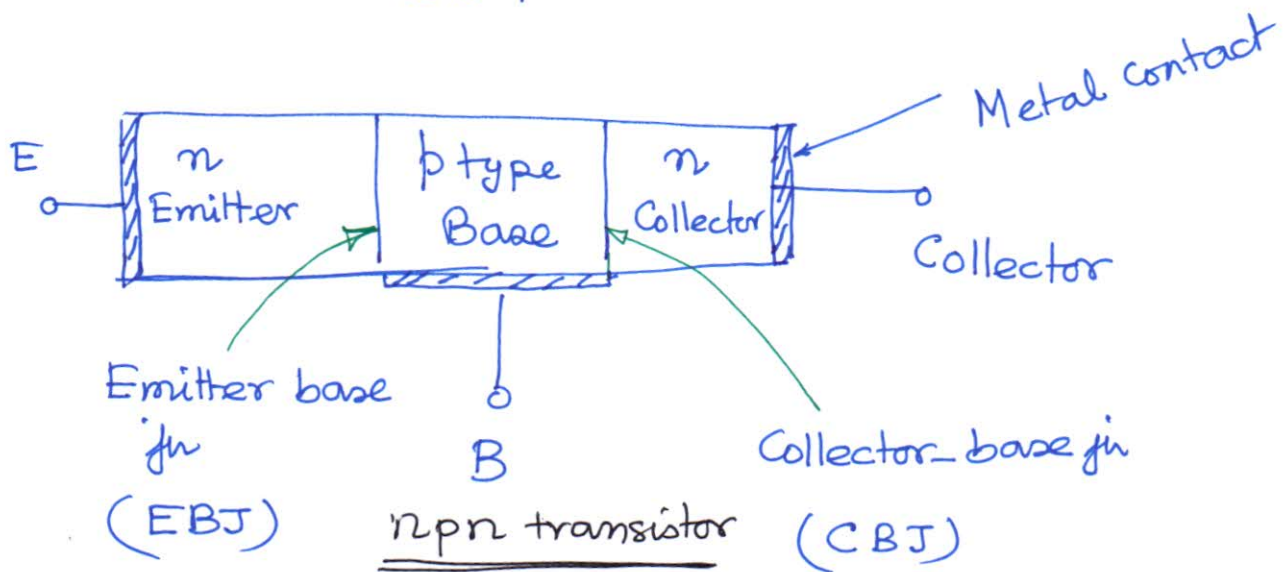


# BIPOLAR JUNCTION TRANSISTOR

1.

## BJT



BJT has three semiconductor regions:

Emitter region (n type)

Base region (p type)


npn transistor

Collector region (n type)

Another transistor pnp has

p type Emitter, n type Base, p type Collector

as shown below

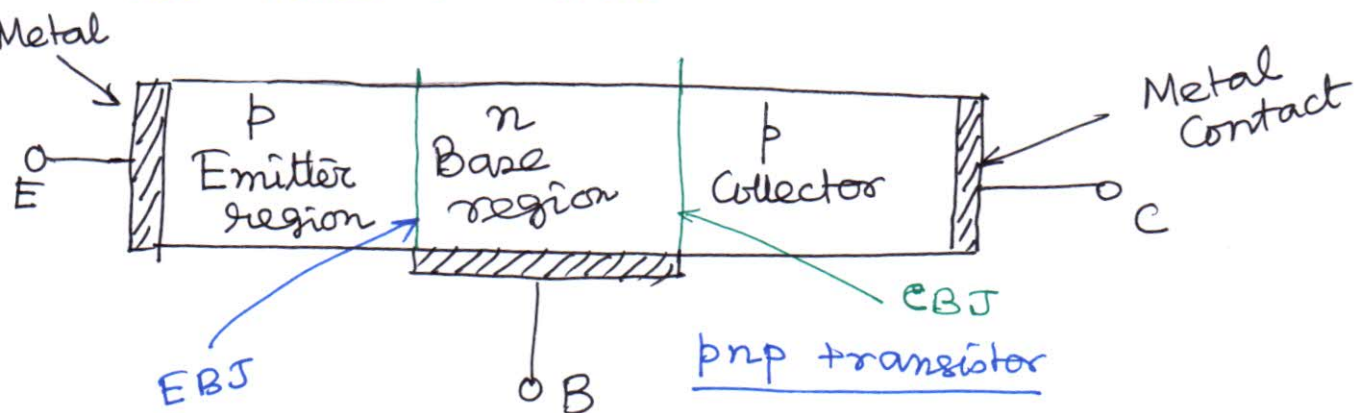

The transistor consists of two pn junctions

(i) EBJ

(ii) CBJ

Depending on the bias condition (forward/reverse) of each of these junctions, different modes of operation of BJT are obtained

Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward


Active Mode : Transistor operates as an amplifier

Switching application (logic circuits) :

Cutoff and saturation mode.

Cutoff mode : No current flows as both junctions are reverse biased.

# Transistor Operation

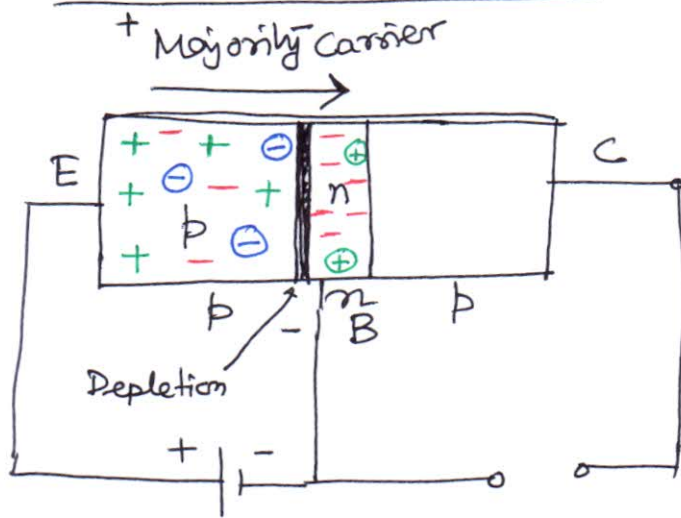


## pnp transistor

No Base to Collector Bias

Emitter to Base  $j_n$  is forward bias

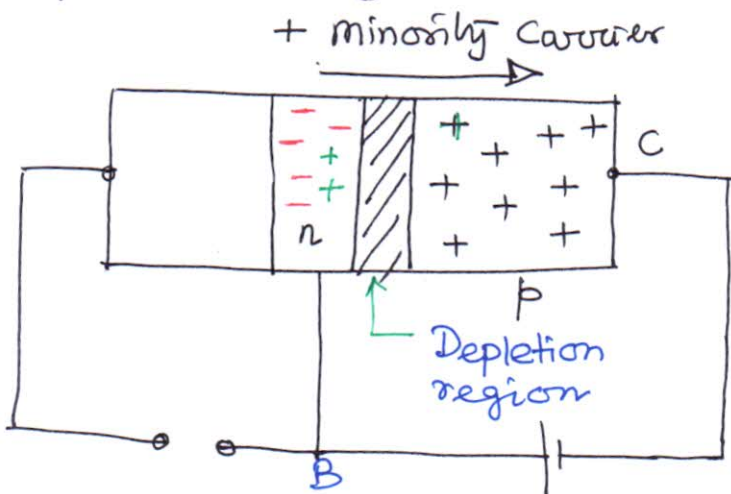
Depletion region is reduced due to forward bias.  $\Rightarrow$  Heavy flow of majority carriers from p to n type material.



Now remove forward Bias (Base-Emitter) and reverse bias Collector Base  $j_n$ .

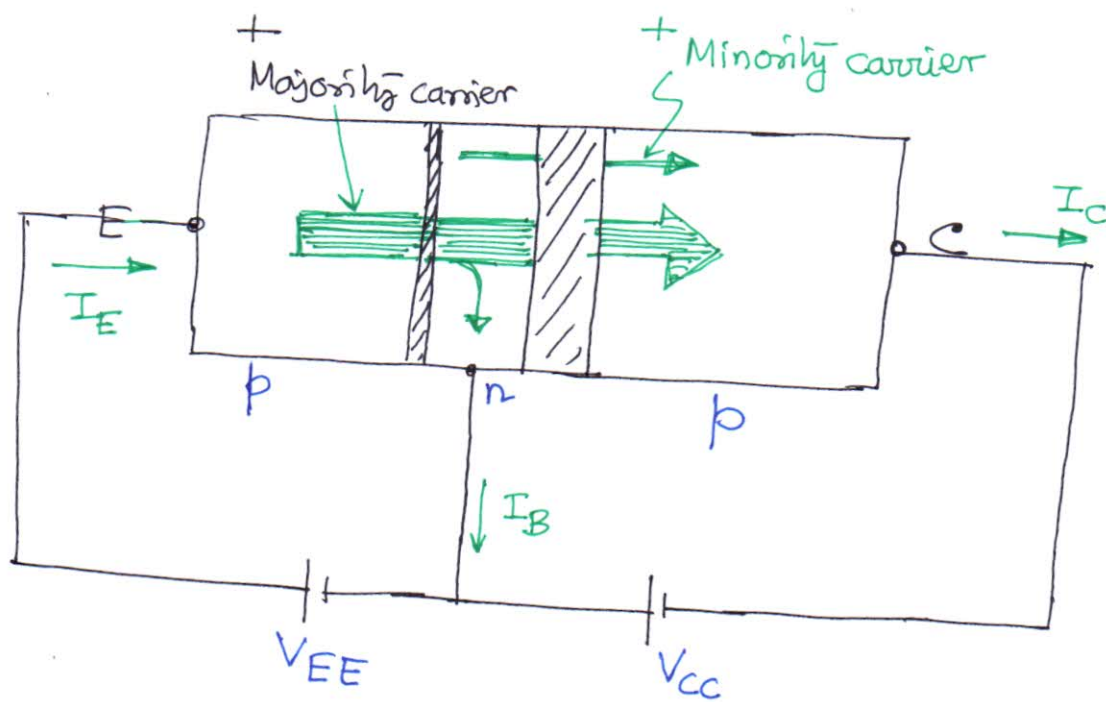Majority carrier flow is zero, only minority carrier flows. Depletion region is widened.





Both biasing potentials have been applied to a pnp transistor, majority and minority carrier flow indicated.

1. A large no. of majority carrier will diffuse across the forward biased p-n junction into n material.
2. Whether these carriers will contribute directly to base current  $I_B$  or pass directly to p type material.
3. Since the sandwiched n type material is very thin, and has a low conductivity, a very small number of these carriers will take this path of high resistance to the base terminal.


The magnitude of base current ( $I_B$ ) is typically on the order of microamperes as compared to milliamp of emitter and collector  $ct$ .

5. The larger number of these <sup>majority</sup> carriers will diffuse across the reverse-biased junction into p type material connected to the collector terminal

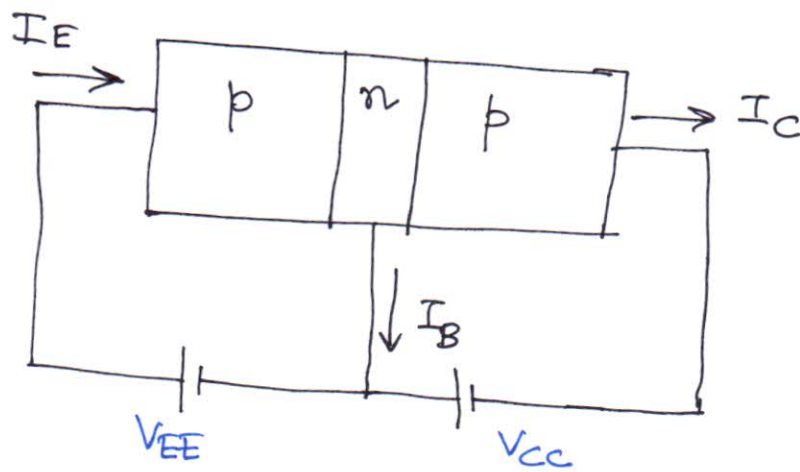6. Note that injected majority carrier from p side (Emitter) becomes minority carriers in the n type material (Base).

Thus there has been an injection of minority carriers into the n type base region.

Combining this with the fact that all the minority carriers in the depletion region will cross the reverse-biased junction of the diode accounts for the flow.



Apply Kirchhoff's current law to the transistor

$$I_E = I_B + I_C$$

The collector current is composed of two components

(i) majority carriers (ii) minority carriers

The minority carrier component is called the leakage current and it is given by  $I_{CO}$

$I_{CO}$  ( $I_C$  current with emitter terminal open)

$$I_C = I_{C \text{ majority}} + I_{CO \text{ minority}}$$


$I_C$  is measured in mA,  $I_{CO}$  in  $\mu A$  or nA.

Like  $I_S$ ,  $I_{CO}$  is temperature sensitive.

It can severely affect the stability at high temp if not considered properly.



# COMMON BASE CONFIGURATION

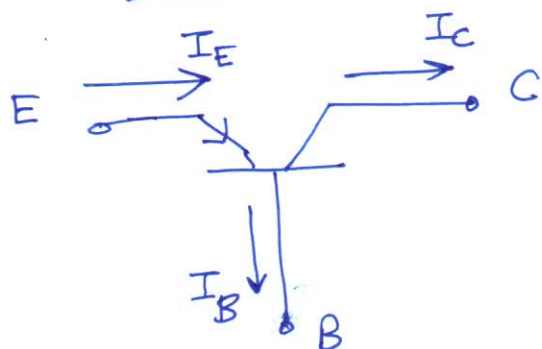


Base is common to both i/p and o/p


The arrow in the graphic symbol defines the direction of emitter current (Conventional flow) through the device.

$$I_E = I_C + I_B$$

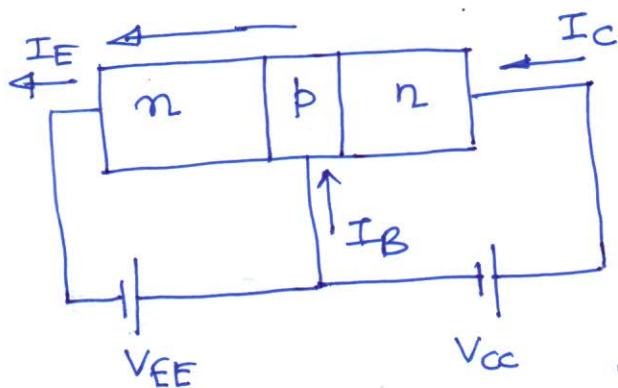Applied bias should be such as to establish current in the direction indicated for each branch.



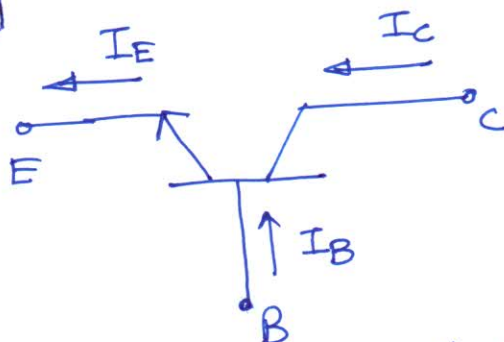
Current flow direction in an npn transistor




input characteristic

$I_E$  (input current) vs  $V_{BE}$  (input voltage)

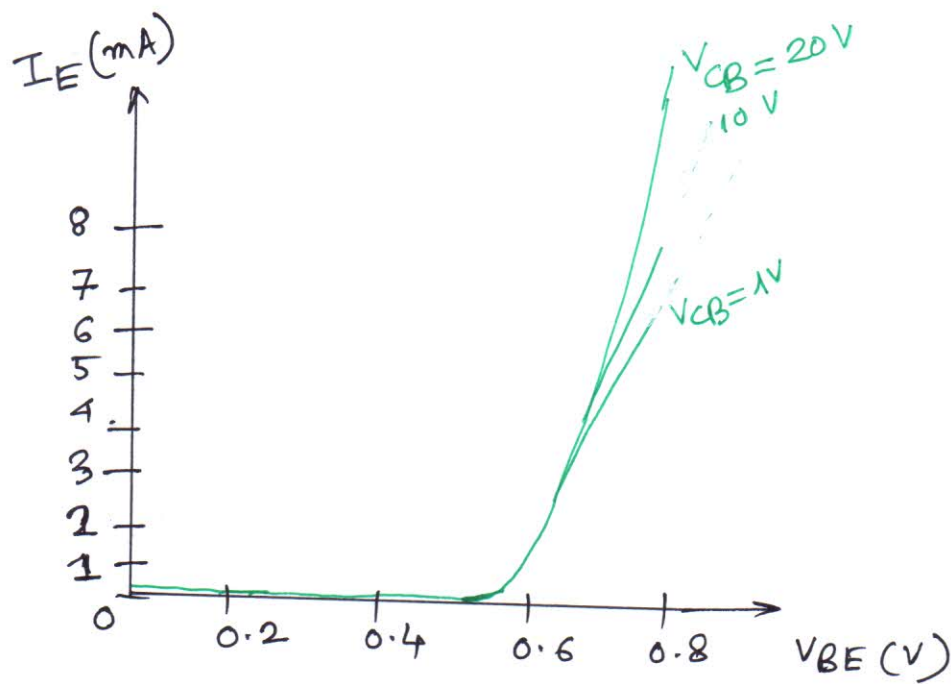for various levels of o/p voltage  $V_{CB}$



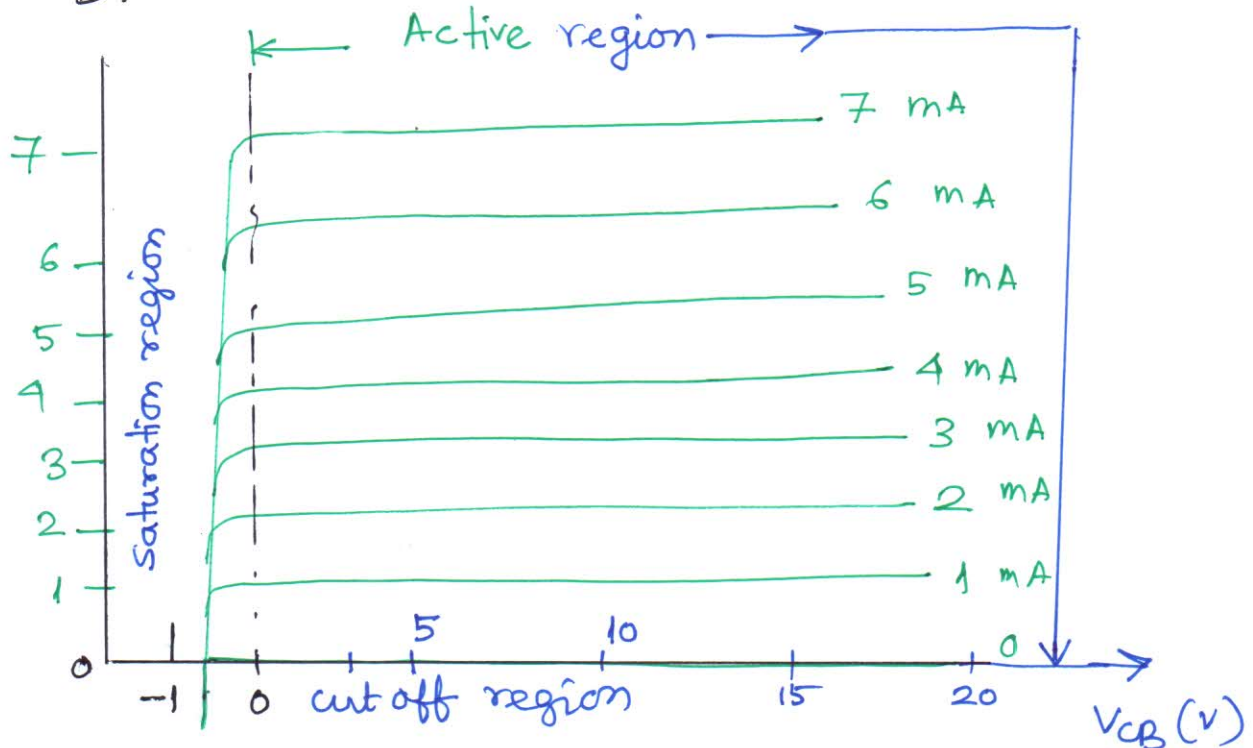i/p characteristics of CB, mode, shows variation of  $I_E$  vs  $V_{BE}$  for various levels of  $V_{CB}$ .



O/p characteristic of CB




O/p characteristics relate output  $I_C$  to an output voltage ( $V_{CB}$ ) for various levels of input current ( $I_E$ ).

Three regions of interest: active, saturation and cutoff.

Active region : CB jn is reverse biased  
EB jn forward biased


used for linear amplification.

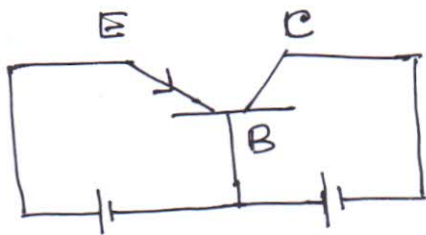

B.E jn is fwd biased  
CB jn is rev biased.

At lower end of active region  $I_E = 0$

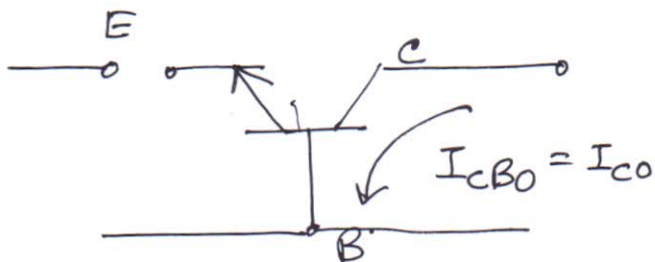$I_C = I_{CO}$   $I_{CO}$  is very small, of the order of  $\mu A$ .



Ckt Condition when  $I_E = 0$ .

$I_{CO}$  is  $I_{CB0}$ .  $I_{CB0}$  is temp dependent

At higher temperature,  $I_{CB0}$  effect may become imp.

- As  $I_E$  increases above zero, collector  $I_C$  increases to a magnitude essentially equal to  $I_E$ .

Effect of  $V_{CB}$  is negligible on collector  $I_C$  for the active region.

Thus in the active region

$$I_C \approx I_E$$

Cutoff region : The region where  $I_C = 0$

In cutoff region, the collector-base  $pn$  and base-emitter  $pn$  both are reverse biased.

Saturation region

The region of characteristic left of  $V_{CB} = 0V$ .  
Note the exponential increase in collector  $I_C$  as voltage  $V_{CB}$  increases toward  $0V$ .


In saturation region the collector-base and base-emitter junctions are forward biased.

## Input characteristics of CB

For fixed values of Collector voltage, as  $(V_{CB})$  base to emitter voltage increases, the emitter current increases in a manner that closely resembles diode characteristic.

Increasing levels of  $V_{CB}$  have such a small effect on characteristics that as a first approximation, the change due to changes in  $V_{CB}$  can be ignored.

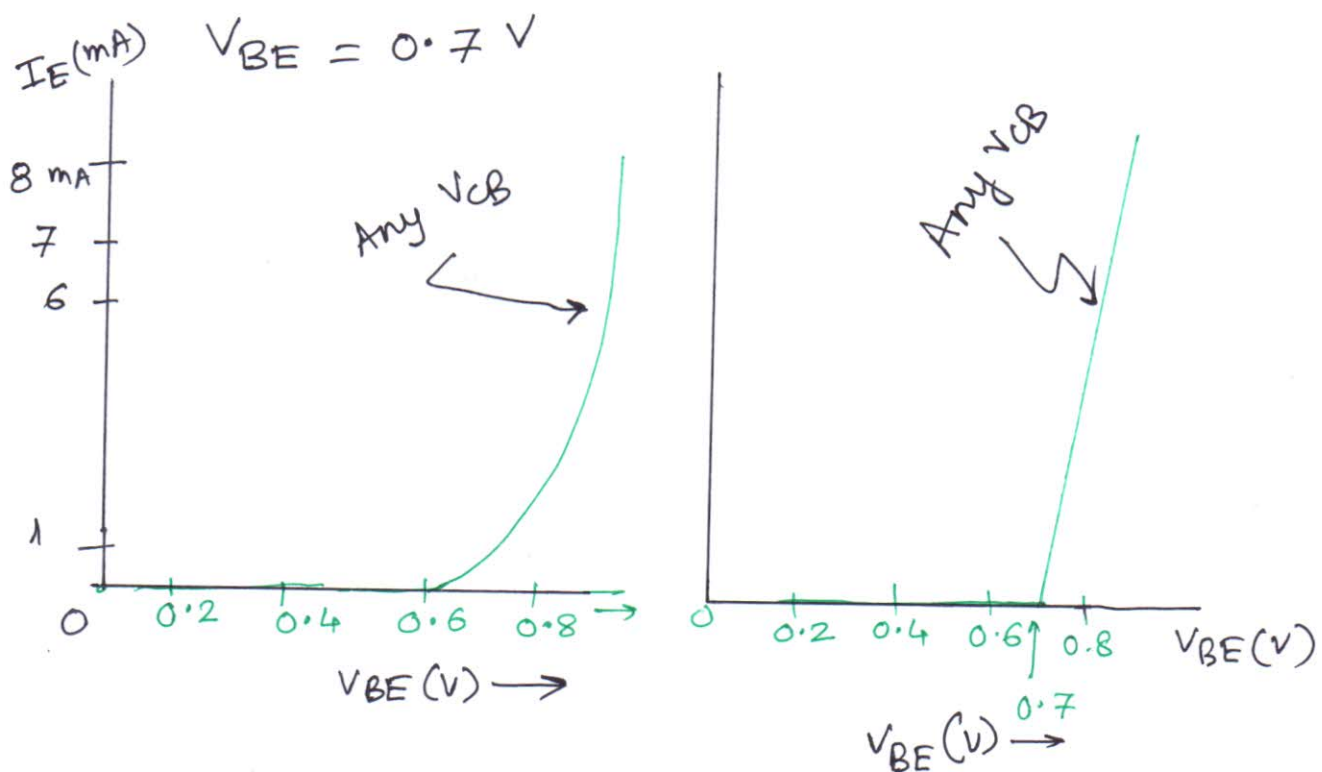Once a transistor is in 'ON' state, the base to emitter voltage will be assumed to be



## Alpha ( $\alpha$ )

In the dc mode, the levels of  $I_C$  and  $I_E$  are due to majority carriers and they are related by a quantity called ' $\alpha$ ', defined as

$$\alpha_{dc} = \frac{I_C}{I_E}$$

$I_C$  &  $I_E$  are levels of current at the point of operation.

Although the characteristics suggest  $\alpha = 1$ , for practical devices, the level of  $\alpha$  typically lies between 0.9 to 0.99

$$I_C = I_{C \text{ majority}} + I_{C \text{ minority}}$$

$$= \alpha I_E + I_{CBO}$$

$$\text{When } I_E = 0, \text{ mA} \quad \underline{I_C = I_{CBO}}$$

But  $I_{CBO}$  is very small,

So when  $I_E = 0 \text{ mA}$ ,  $I_C$  appears to be 0 mA in the figure.



For ac situations, where the point of operation moves on the characteristic curve,


then an ac alpha is defined by

$$\alpha_{ac} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CB} \text{ const}}$$

Common base short ckt amplification factor
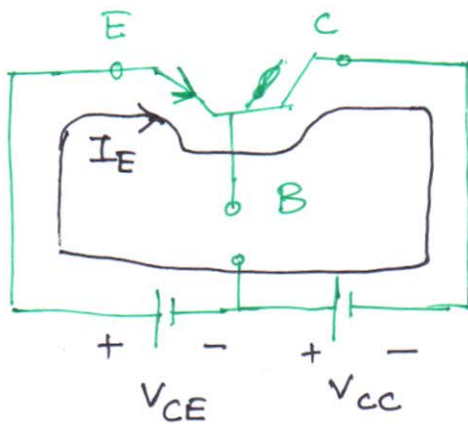
### Biasing


Proper biasing of common-base configuration in the active region can be determined quickly using  $I_C \cong I_E$  and assuming for the moment that  $I_B \cong 0 \mu A$



The arrow of the symbol defines the direction of conventional flow for  $I_E \cong I_C$

PNP transistor

## Transistor Amplifying Action

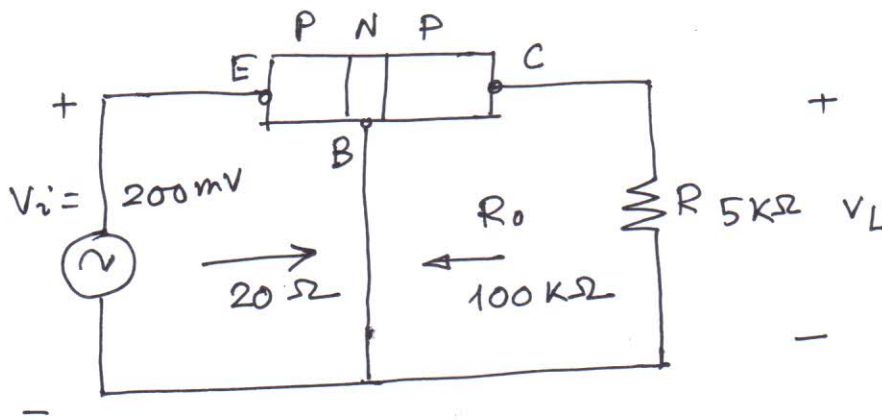

We do not show biasing as we are interested in ac operation.

i/p resistance is determined by i/p characteristic  $I_E$  vs  $V_{BE}$  (that of a typically fwd biased diode).

o/p resistance determined by o/p characteristic (More horizontal the curves, higher the resistance) typically  $50 \text{ k}\Omega$  to  $1 \text{ M}\Omega$ .

$$I_i = \frac{V_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA}$$

$$\alpha_{AC} = 1, \quad I_e = I_i = 10 \text{ mA}$$

$$I_L = I_c \simeq I_e = 10 \text{ mA}$$

$$V_L = I_L \cdot R = (10 \text{ mA}) \cdot 5 \text{ k}\Omega = 50 \text{ V}$$

### Amplification Factor

$$A_v = \frac{V_L}{V_i} = \frac{50V}{200mV} = 250$$

Typical values for voltage amplification for Common base Configuration vary from 50 to 300.

The current amplification is always less than 1 for CB Configuration.

Thus the basic amplifying action is produced by transferring a current  $I$  from a low to high resistance ckt.

transfer + resistor  $\Rightarrow$  transistor